

Basics of Electrical & Electronics Engineering

UNIT 4

BJT applications/Feedback amplifier



TRANSISTORS



INTRODUCTION :-

- ❖ Transistor was invented by William Shockley in 1947.
- ❖ Invention of transistor made the electronic circuits smaller, more efficient & less expensive.
- ❖ Transistor has a very important property that it can raise (Increase) the strength of a weak signal. This property is called **amplification**.

Transistor :-


A transistor consists of two PN junctions. The junctions are formed by sandwiching either P-type or N-type semiconductor layers between a pair of opposite types as shown below. Transistors are of two types.

1) NPN Transistor :-

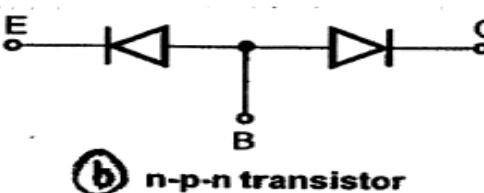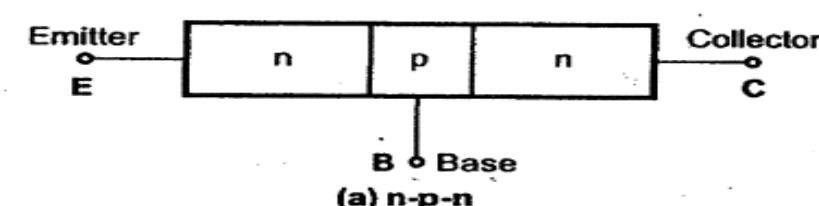

(b) n-p-n transistor


Fig. Two-diode transistor analogy

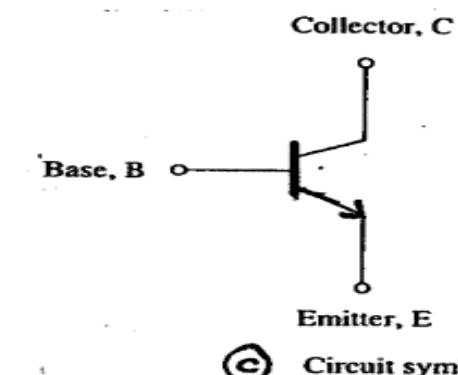


(c) Circuit symbol




2) PNP Transistor :-

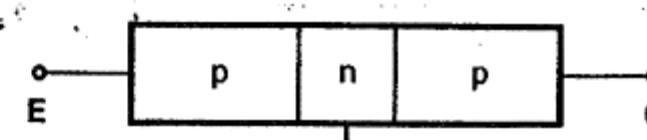

(a) p-n-p

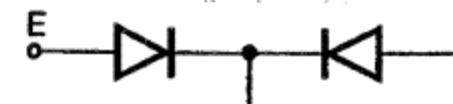

(b) p-n-p transistor

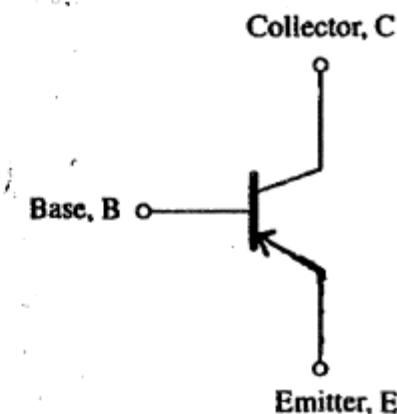

(c)

Circuit symbol



Transistors Classification :-

Transistors are classified into two types :

1) Unipolar Junction Transistors (UJT) :-

In UJT, current conduction is only due to one type of charge carriers, that to majority carriers.

2) Bipolar Junction Transistors (BJT) :-

In BJT, current conduction is due to both the type of charge carriers i.e holes & electrons are the majority & minority carriers.

Transistor Terminals :-

Transistor terminals are Emitter, Base & Collector.

❖ Emitter (E):-

- ◆ Emitter is heavily doped than other two regions. Its function is to supply majority carriers (either electrons or holes) to the other two regions.
- ◆ Emitter is always forward biased w.r.to base.

❖ Base (B):-


- ◆ It is the middle region that forms two P-N junctions in the transistor.
- ◆ The base is lightly doped & much thinner than the emitter & collector region.

❖ Collector (C):-

- ◆ It is a region situated in the other side of transistor(i.e. the side opposite to the emitter), which collects charge carriers(i.e. holes & electrons).
- ◆ The collector of a transistor is always larger than the emitter & base of a transistor.




Transistor Junctions :-

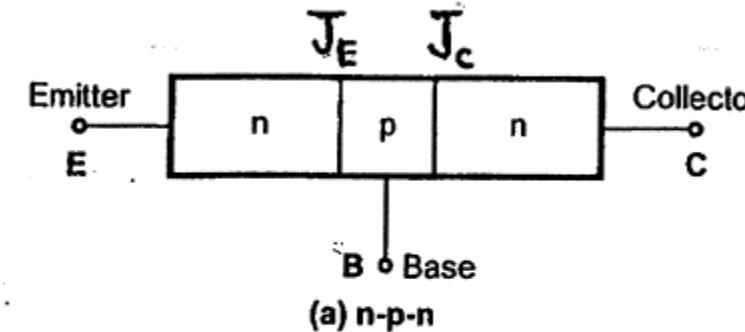

The transistor has two PN junctions J_E & J_C as shown in figure. The junction J_E is a junction between emitter & base regions. Thus it is known as emitter-base junction.(Forward Biased).


Similarly, the junction J_C is a junction between collector & base regions. Thus it is known as Collector-base junction.(Reversed Biased).

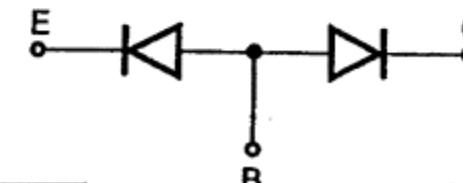Thus transistor is like two PN junction diodes connected back to back as shown in figure 2.





Origin of the name “Transistor” :-

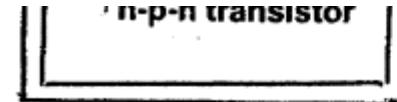

- As we know transistor has two PN junction. One junction is forward biased & the other is reverse biased.
- The forward bias junction has a low resistance path where as reverse biased junction has a high resistance path.
- The weak signal is introduced in the low resistance circuit & output is taken from the high resistance circuit.
- Therefore, a transistor transfers a signal from a low resistance to high resistance & consequently name transistor is given by

TRANSfer + resISTOR = TRANSISTOR




Unbiased NPN Transistor :-

- ❖ Draw a block diagram of an unbiased NPN transistor. Identify each part of the device and show the depletion regions & barrier voltages.
Briefly explain.

Jan-10,5M

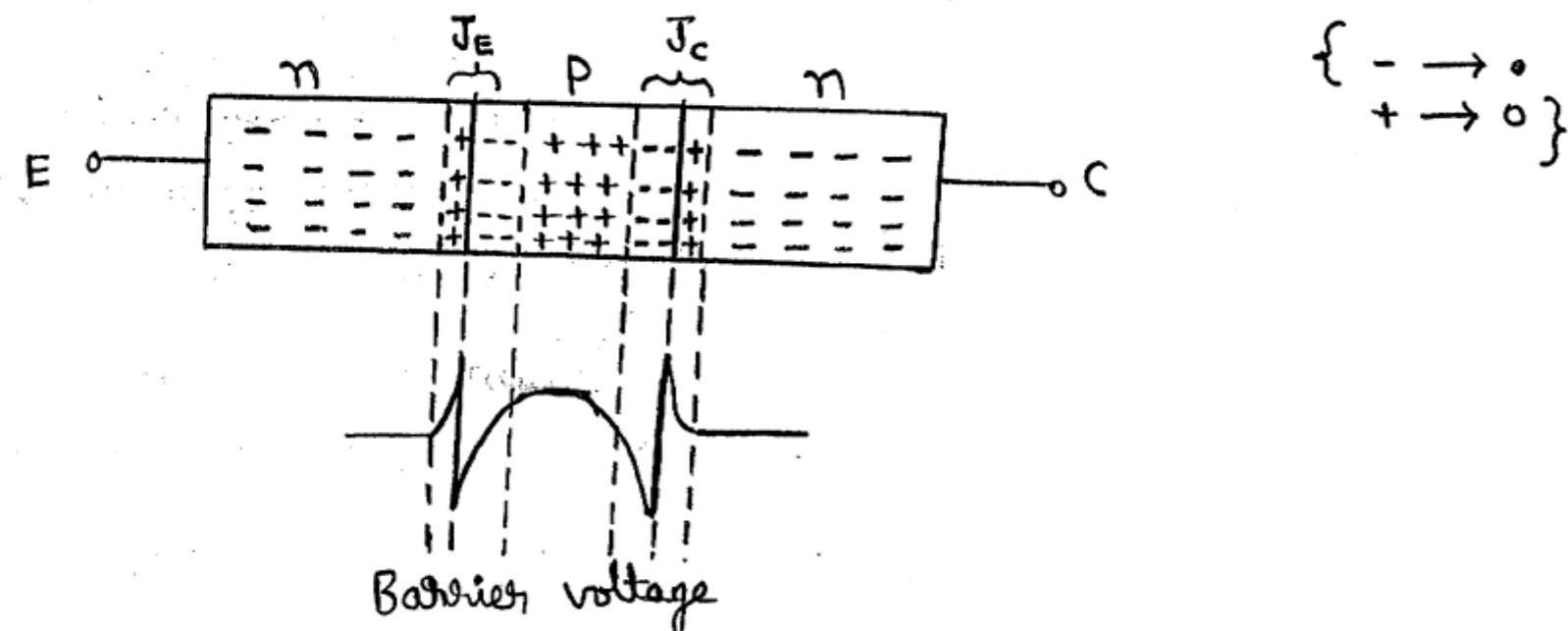An unbiased transistor means a transistor with no external voltage is applied. Thus no current flows in any of transistor leads.



- ❖ During diffusion process, depletion region penetrates more deeply into the lightly doped base. The depletion region at emitter junction penetrates less in the heavily doped emitter.
- ❖ Similarly, the depletion region at collector junction penetrates less in the heavily doped collector and extends more in the base region.
- ❖ Thus depletion layer width at the collector junction is more than the depletion layer width at the emitter junction.
- ❖ For silicon transistor barrier voltage is 0.7V & 0.3V for germanium transistor.



Transistor operation :-

i) Operation of NPN transistor :-

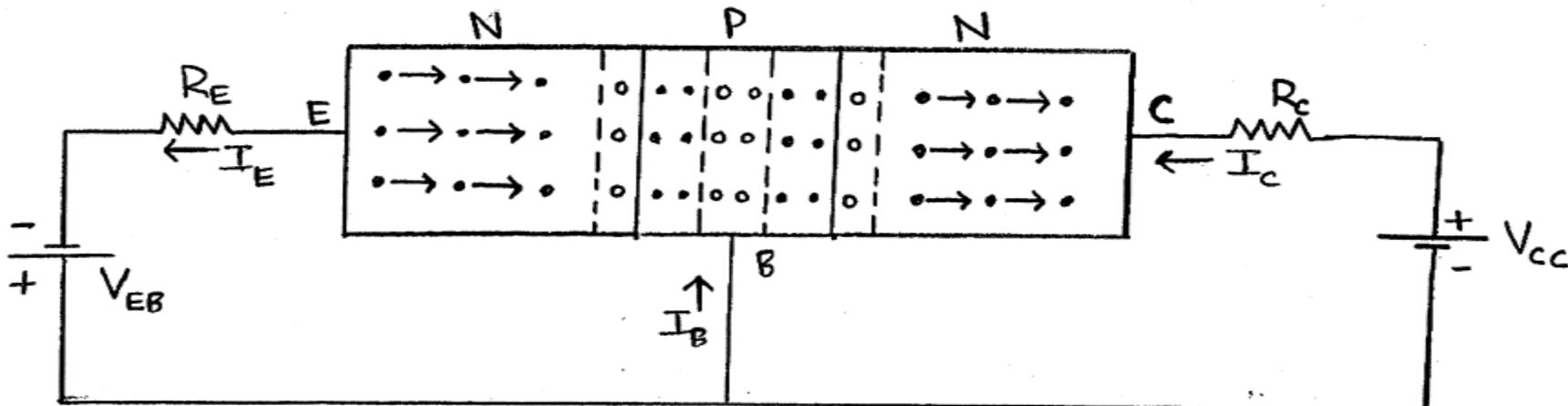


Fig ①: operation of NPN transistor

Figure 1 shows an NPN transistor biased in active mode.

- ❖ In NPN transistor current is due to the movement of free electrons. The emitter to base of a transistor is forward biased & collector to base junction is reversed biased.
- ❖ When V_{EB} is greater than barrier potential ($V\gamma$), emitter to base junction is forward biased causes the free electrons in the N-type emitter to flow towards the base region. This constitutes the emitter current I_E .

- ❖ As base is lightly doped, only few electrons combine with the holes & constitute base current I_B . Thus most of the electrons will diffuse to the collector region & constitutes collector current I_c .
- ❖ There is another component of collector current due to thermally generated carriers. This current component is called reverse saturation current & is quite small.
- ❖ The emitter current is given by $I_E = I_B + I_c$

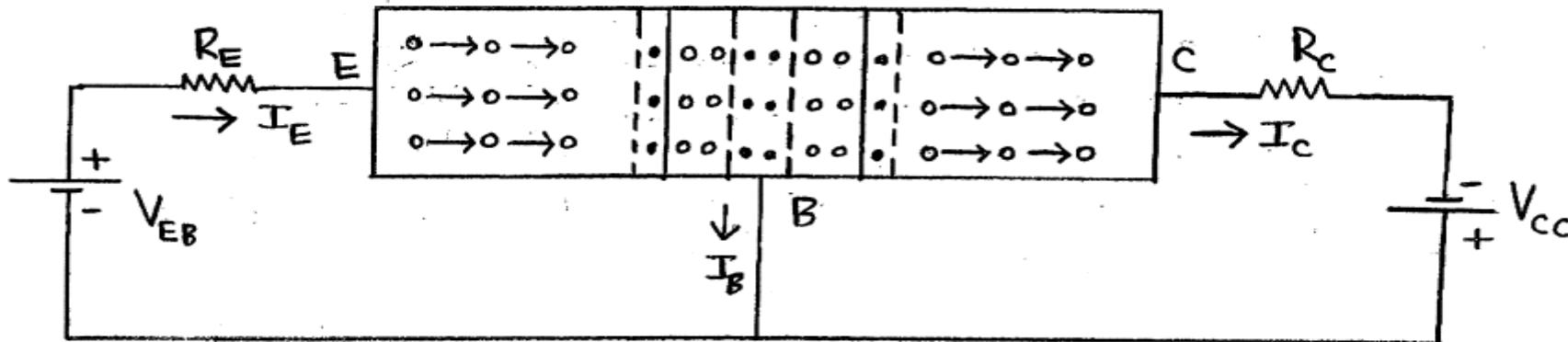


Fig ①: operation of PNP transistor

- ❖ Figure 1 shows an PNP transistor biased in active mode. In PNP transistor current is due to the movement of holes. The emitter to base junction is forward biased & collector to base junction is reversed biased.
- ❖ When V_{EB} is greater than barrier potential ($V\gamma$), emitter to base junction is forward biased causes the holes in the emitter region to flow towards the base region. This constitutes the emitter current I_E .
- ❖ As base is lightly doped only few holes combines with the holes & constitute base current ' I_B '. Thus most of the holes will diffuse to the collector region & constitutes collector current ' I_C '.

- ❖ There is another component of collector current due to thermally generated carriers. This current component is called reverse saturation current & is quite small.
- ❖ The emitter current is given by $I_E = I_B + I_C$



Transistor Currents :- (PNP)

- ❖ Sketch & explain the current components crossing each junction of a transistor biased in the active region.

Jan-04,6M, Jan-03,5M

- ❖ With a neat sketch, clearly show the various current components in a PNP transistor & hence establish the relevant equations.

June-04,6M Jan-05,10M Jan-06,7M Jan-07,6M

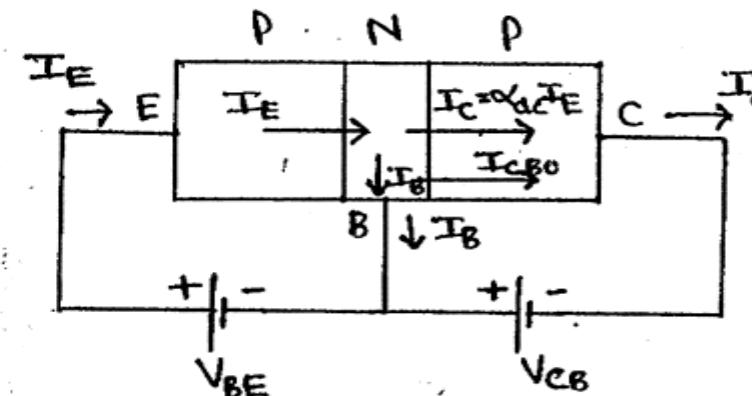


Fig ①: Currents in a PNP Transistor



- * In Fig ①, the current flowing into the emitter terminal is referred to as a emitter Current ' I_E '.
- * Base current ' I_B ' & collector current ' I_C ' both flow out of the transistor, while ' I_E ' flows into the transistor.

$$\therefore I_E = I_B + I_C \rightarrow ①$$

- * Almost all of emitter current ' I_E ' crosses to the collector & only a small portion flows out of the base terminal.
Typically 96.% to 99.5.% of I_E flow across the collector to base junction to become collector current.

$$I_C = \alpha_{dc} I_E \rightarrow ②$$

W.R.T
 $\alpha_{dc} = \frac{I_C}{I_E}$



Where α_{dc} is the emitter to collector current gain & is typically 0.96 to 0.995.

Thus, the collector current is almost equal to the emitter current i.e. $I_c \approx I_E$.

* When C-B junction is reverse biased, a very small reverse saturation current ' I_{CBO} ' flows across the junction, called collector to base leakage current ' I_{CBO} ' & it is very small & can be neglected.

* From eq ① & ②

$$I_E = I_B + I_C \longrightarrow ①$$

$$I_C = \alpha_{dc} I_E \longrightarrow ②$$



Substituting eq ① in eq ②

$$I_C = \alpha_{dc} [I_B + I_c]$$

$$I_c = \alpha_{dc} I_B + \alpha_{dc} I_c$$

$$\alpha_{dc} I_B = \underline{I_c} - \underline{\alpha_{dc} I_c}$$

$$\alpha_{dc} I_B = I_c [1 - \alpha_{dc}]$$

$$I_c = \frac{\alpha_{dc}}{1 - \alpha_{dc}} I_B$$

$$I_c = \beta_{dc} I_B$$

Where, $\beta_{dc} = \alpha_{dc} / 1 - \alpha_{dc}$



β_{dc} is the base to collector current gain.

Typical β_{dc} ranges from 25 to 300. β_{dc} is also termed as common emitter dc current gain. It is also called as h_{FE} .



❖ Draw a sketch to show the various current components in a NPN transistor & deduce the relation between various current components.

Jan-08,8M

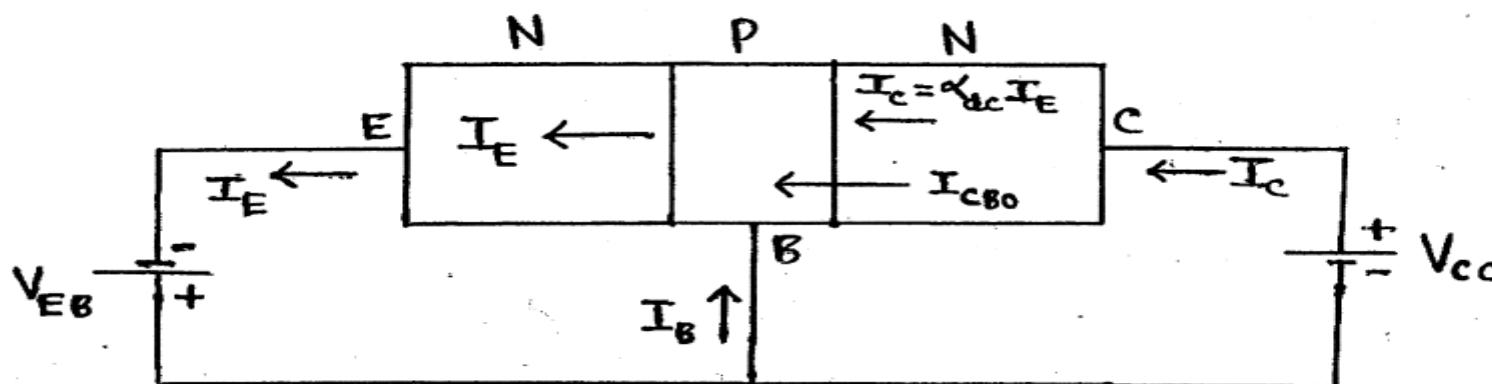


Fig ①: Currents in a NPN Transistor

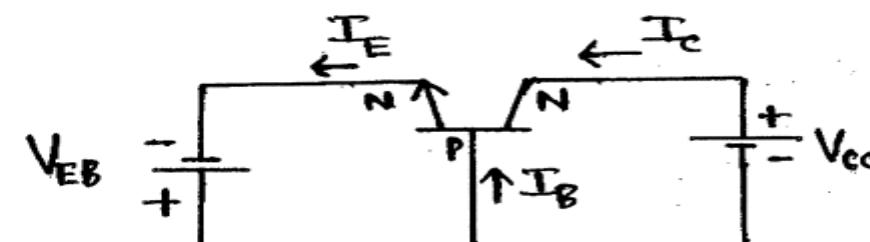


Fig ② : Currents in a NPN Transistor.



* In NPN transistors, electrons are injected into the base.

These electrons constitute the emitter current ' I_E '.

* Assume that 100 electrons are injected into the base region. Since the base is very thin, only few electrons say 2 in number, recombine with the holes. This constitute the base current ' I_B '. The remaining 98 electrons cross the base-collector, constituting collector current ' I_C '.

$$\therefore I_E = I_B + I_C \rightarrow ①$$

WKT $\alpha_{dc} = \frac{I_C}{I_E}$

$$I_C = \alpha_{dc} I_E \rightarrow ②$$

α_{dc} is the emitter-collector current gain & is typically 0.96 to 0.995.

Thus

$$I_C \approx I_E$$



- * When collector-base junction is reverse biased, a very small reverse saturation current (I_{CBO}) flows across the junction, called collector-to-base leakage current ' I_{CBO} ' & it is very small & can be neglected.
- * Substituting eq ① in eq ②, we get

$$I_C = \alpha_{dc} [I_B + I_c]$$

$$\overbrace{I_c}^{\leftarrow} = \alpha_{dc} I_B + \alpha_{dc} I_c$$

$$I_c - \alpha_{dc} I_c = \alpha_{dc} I_B$$

$$I_c [1 - \alpha_{dc}] = \alpha_{dc} I_B$$

$$I_C = \frac{\alpha_{dc}}{1-\alpha_{dc}} \cdot I_B$$

$$I_C = \beta_{dc} I_B$$

Where $\beta_{dc} = \frac{\alpha_{dc}}{1-\alpha_{dc}}$

* β_{dc} is the base - collector current gain: Typically β_{dc} ranges from 25 to 300.



Amplification :-

Current Amplification :-

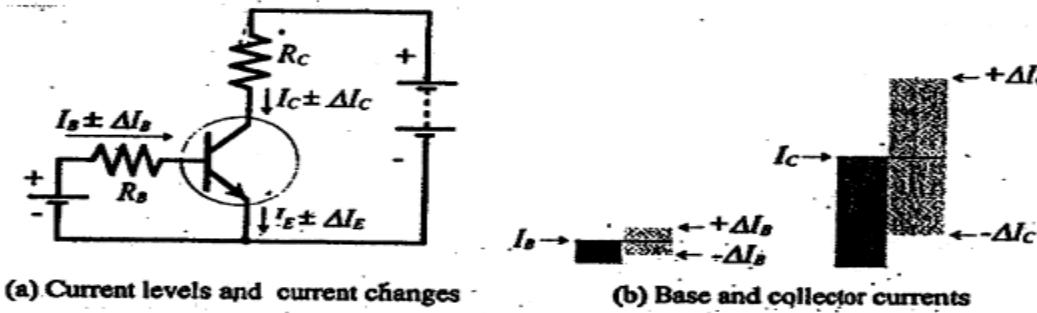


Figure
Increasing and decreasing I_B levels
produces much larger changes in
 I_C and I_E

- * A small change in the base current ΔI_B produces a large change in collector current ΔI_C & a large emitter current change ΔI_E

i.e.
$$\beta_{dc} = \frac{\Delta I_C}{\Delta I_B}$$

- * The common emitter ac current gain is given by

$$\beta_{ac} = \frac{I_C}{I_B}$$

* β_{ac} is also referred to as h_{FE} .



Voltage Amplification :-

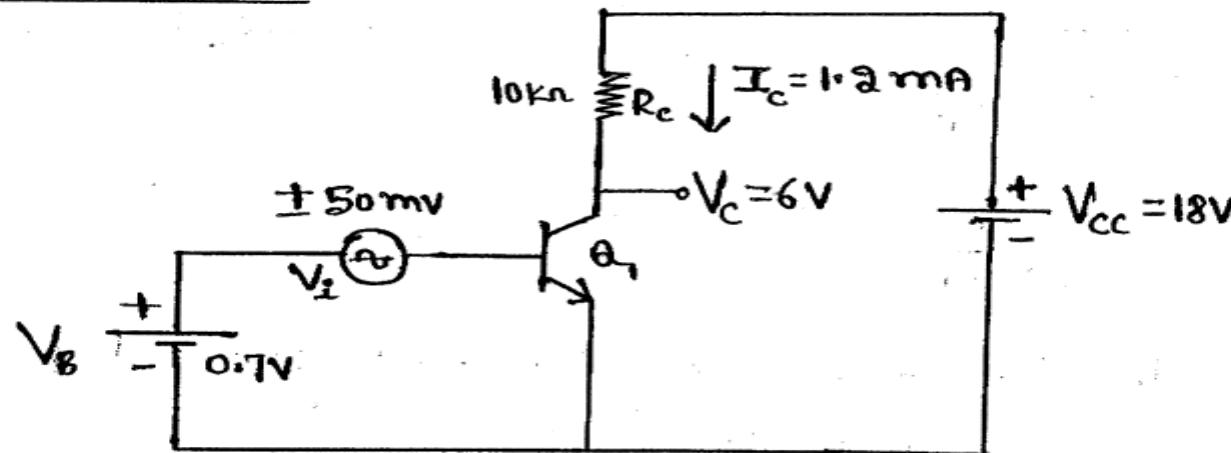


Fig ① : Transistor CE

- * In Fig ①, assume that the transistor Q_1 has $\beta_{ac} = \beta_{dc} = 80$. Note that the $0.7V$ dc voltage source ' V_B ' forward biases the transistor base-emitter junction.
- * An ac Signal ' V_i ' in Series with ' V_B ' provides a $\pm 50\text{mV}$ I/p voltage.
- * The Transistor Collector is connected to a $18V$ dc voltage Source V_{CC} via the $10\text{k}\Omega$ collector Resistor R_C .




* If Q₁ has the I_B/V_{BE} characteristics shown in fig (a), the 0.7V level of V_B produces a 15 μA base current.

i.e. $I_B = 15 \mu A$ for $V_B = 0.7V$

$$I_C = \beta_{dc} I_B = 80 \times 15 \mu A$$

$$\boxed{I_C = 1.2 \text{ mA}}$$

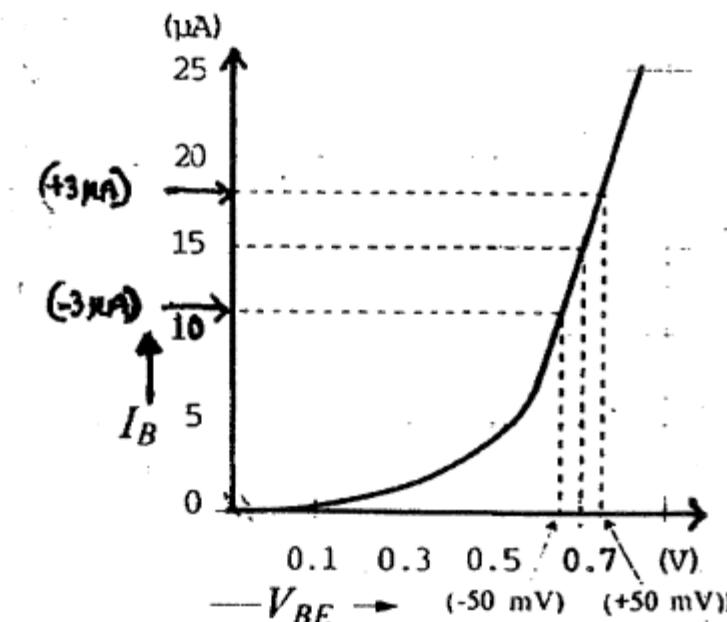

(b) V_{BE} I_B characteristic for Q_1 .



* Applying KVL to Collector-emitter loop

$$V_{cc} - I_c R_c - V_c = 0$$

$$\begin{aligned}V_c &= V_{cc} - I_c R_c \\&= 18V - (1.2mA \times 10k\Omega)\end{aligned}$$

$$\boxed{V_c = 6V}$$

* From Fig ②

$$I_b = \pm 3\mu A \text{ for } V_i = \pm 50mV$$

$$I_c = \beta_{ac} I_b = 80 \times (\pm 3\mu A)$$

$$I_c = \pm 240\mu A$$

* $V_o = I_c R_C$

$$V_o = \pm 240\mu A \times 10k\Omega$$



$$V_o = \pm 240 \mu A \times 10 k\Omega$$

$$V_o = \pm 2.4 V$$

$$* A_v = \frac{V_o}{V_i} = \frac{\pm 2.4 V}{\pm 50 mV}$$

$$A_v = 48$$



❖ Obtain the relationship between α_{dc} & β_{dc} . Jan-11,4M | jan-09,4M

WKT

$$I_E = I_B + I_C \rightarrow ①$$

Dividing on both sides of eq ① by I_C

$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + \frac{I_C}{I_C}$$

$$\frac{I_E}{I_B} = \frac{I_B}{I_C} + 1 \rightarrow ②$$

WKT

$\beta = I_C/I_B$	$\alpha = I_C/I_E$
$\gamma_B = I_B/I_C$	$\gamma_\alpha = I_E/I_C$

Then eq ② becomes

$$\gamma_\alpha = \gamma_B + 1$$



$$\frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\frac{1}{\alpha} = \frac{1+\beta}{\beta}$$

$$\therefore \boxed{\alpha = \frac{\beta}{1+\beta}} \rightarrow ③$$

Eq ③ can be written as

$$\alpha(1+\beta) = \beta$$

$$\alpha + \alpha\beta = \beta$$

$$\alpha = \beta - \alpha\beta$$

$$\alpha = \beta[1 - \alpha]$$

$$\boxed{\beta = \frac{\alpha}{1-\alpha}}$$



❖ Obtain the relationship between α & γ .

WKT

$$\gamma = \frac{I_E}{I_B} \rightarrow ①$$

Multiply & divide eq ① by I_C

$$\gamma = \frac{I_E}{I_B} \cdot \frac{I_C}{I_C}$$

$$\gamma = \frac{I_E}{I_C} \cdot \frac{I_C}{I_B}$$

WKT

$$\beta = \frac{I_C}{I_B} \quad \& \quad \frac{1}{\alpha} = \frac{I_E}{I_C}$$

$$\gamma = \frac{1}{\alpha} \cdot \beta$$

$$\gamma = \frac{\beta}{\alpha} \rightarrow ②$$

Eq ② can be written as

$$\therefore \alpha = \frac{\beta}{1+\beta}$$



Eq ② can be written as

$$\gamma = \frac{\beta}{\frac{\beta}{1+\beta}}$$

$$\gamma = 1 + \beta$$

$$\boxed{\gamma \approx \beta}$$



Total Collector Current :-

❖ Obtain the expression for the collector current for an npn or pnp transistor.

$$\text{WKT} \quad I_c = \alpha I_E + I_{CBO}$$

$$I_c = \alpha [I_B + I_c] + I_{CBO}$$

$$I_c = \alpha I_B + \cancel{\alpha I_c} + I_{CBO}$$

$$I_c - \cancel{\alpha I_c} = \alpha I_B + I_{CBO}$$

$$I_c [1 - \cancel{\alpha}] = \alpha I_B + I_{CBO}$$

$$I_c = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$I_c = \beta I_B + (1+\beta) \cdot I_{CBO}$$

Where $I_{CEO} = (1+\beta) I_{CBO}$

$$I_c = \beta I_B + I_{CEO}$$

NOTE:-

$$\text{WKT } \alpha = \frac{\beta}{1+\beta}$$

$$1-\alpha = 1 - \frac{\beta}{1+\beta}$$

$$1-\alpha = \frac{1+\beta-\beta}{1+\beta}$$

$$1-\alpha = \gamma_{1+\beta}$$

$$\boxed{\frac{1}{1-\alpha} = 1+\beta}$$



Transistor as an Amplifier :-

- ❖ A transistor is capable of providing amplification. Explain the basic transistor amplifier with suitable diagrams.

June-03,6M

- ❖ Show that a transistor could be used as an amplifier.

June-06,5M June-08,6M

- ♣ A transistor increases the strength of the weak signal acting as an amplifier.

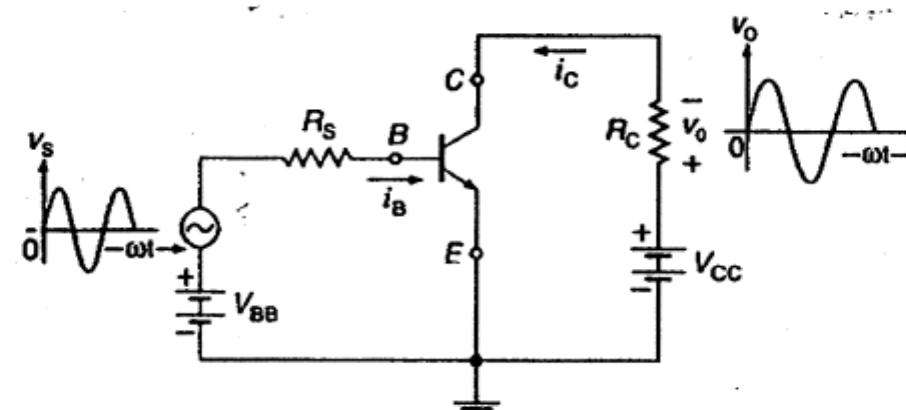


Fig. Basic common emitter amplifier.



- ◆ Figure shows basic transistor circuit of an amplifier. The supply voltage V_{BB} forward biases the emitter to base junction & V_{CC} reverse biases the collector to base junction. Thus transistor operates in active region.
- ◆ The magnitude of the ac input signal is such that it always forward bias the emitter to base junction regardless of the polarity of the ac input signal.
- ◆ During **+ve half cycle** of the input signal, the forward bias across the emitter to base junction is increased, which increases the collector current. The increased collector current **produces greater voltage drop across the resistance 'R_C'**.
- ◆ During **-ve half cycle** of the input signal, the forward bias across the emitter to base junction is decreased, which decreases the

collector current. The decreased collector current ***produces smaller voltage drop across the resistance 'Rc'.***

- ◆ The small ac input signal produces a large ac output signal. Thus the transistor acts as an amplifier.



TRANSISTOR BIASING :-

The application of dc voltages across the transistor terminals is called biasing.

There are three modes of transistor operation.

SL No	Mode	Emitter-base junction	Collector-base junction
1	Active	Forward	Reverse
2	Saturation	Forward	Forward
3	Cut-off	Reverse	Reverse

NOTE:- The modes of operation are same for both NPN & PNP transistor.

For common-base configuration




Transistor Configurations :-

Transistor has three terminals namely **Emitter (E)**, **Base(B)** & **Collector(C)**. When a transistor is connected in a circuit, we require four terminals i.e. two terminals for input and two for output.


Thus out of three terminals, **one terminal is made common to both input and output terminals.**

There are three different types of configurations or connection :

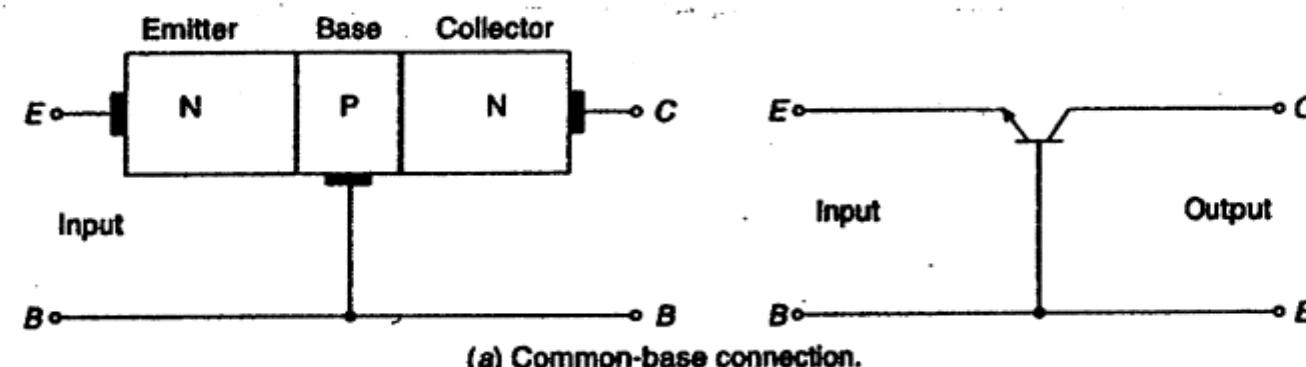
- 1) Common-Base Configuration (**CB**)
- 2) Common-Emitter Configuration (**CE**)
- 3) Common-Collector Configuration (**CC**)



(a) Common-base connection.

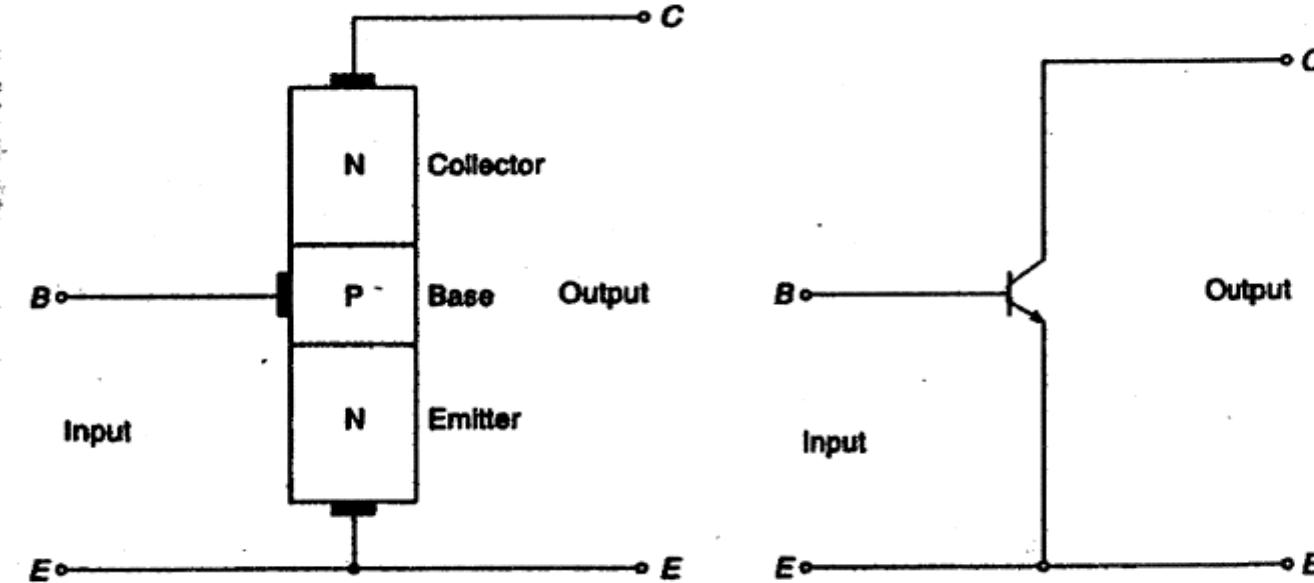

(b) Common-emitter connection.

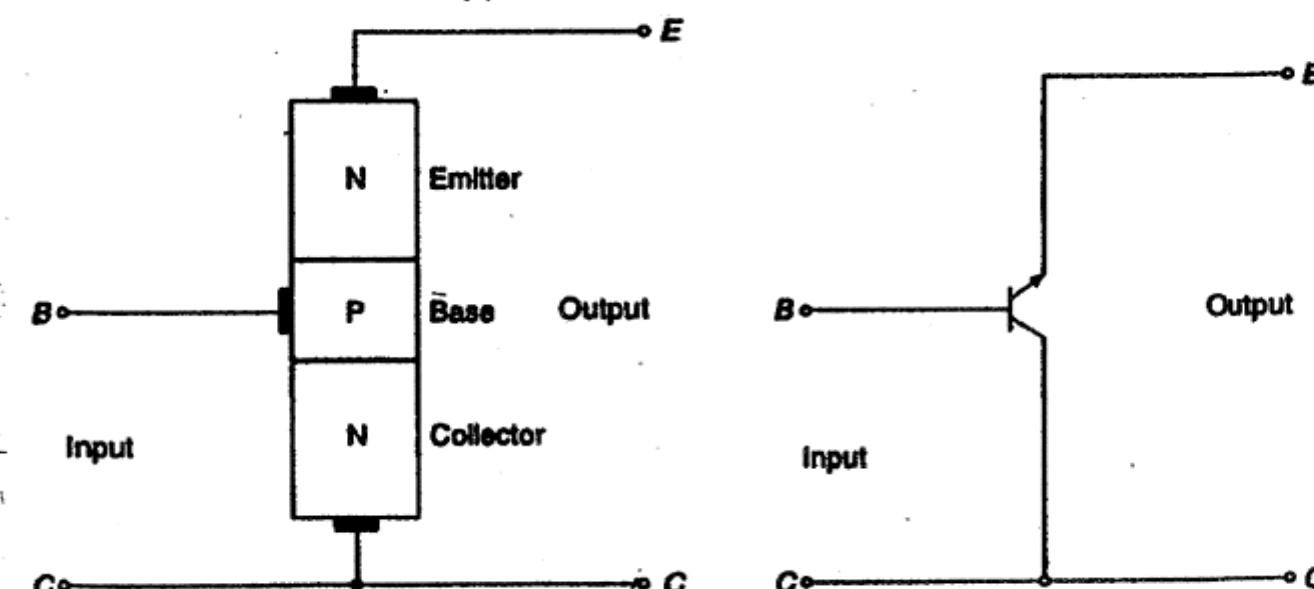

(c) Common-collector connection.


Fig. Transistor circuit connections or configurations.





- * Explain the input and output characteristics for a CE configuration BJT circuit. Discuss each region on the characteristics.


I_c Jan - II, 6M (OLD)

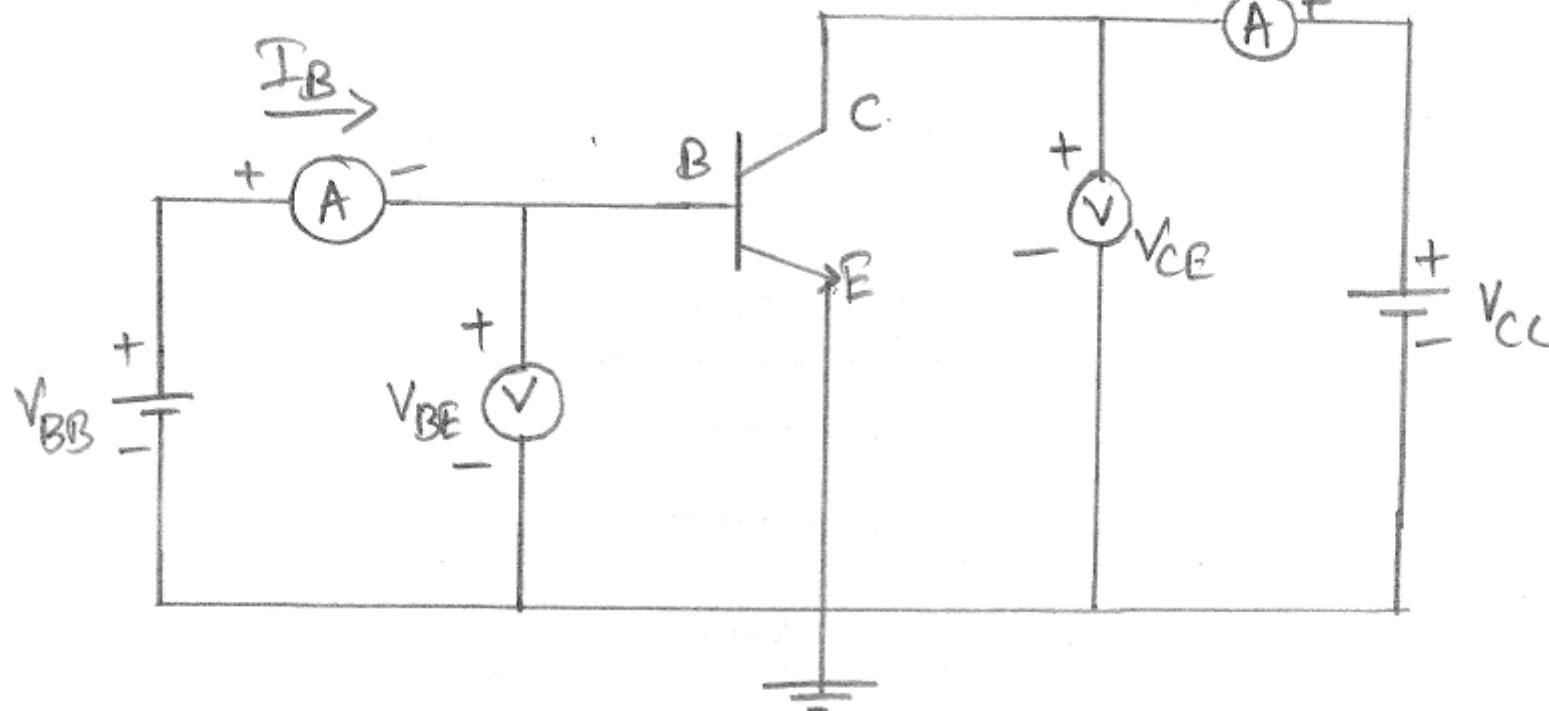

Fig① : ckt for determining transistor common emitter characteristics



- * These curves give the relationship b/w the base current I_B & the base emitter voltage V_{BE} for a constant collector emitter voltage V_{CE} .
- * To obtain I_{BP} characteristic, the o/p voltage 'V_{CE}' is kept constant, I_{BP} voltage 'V_{BE}' is varied in small intervals & the corresponding change in I_{BP} current 'I_B' is recorded.
- * I_B is then plotted against V_{BE} as shown in fig⑤. The experiment is repeated for other values of 'V_{CE}' say 2V, 6V, ... etc.

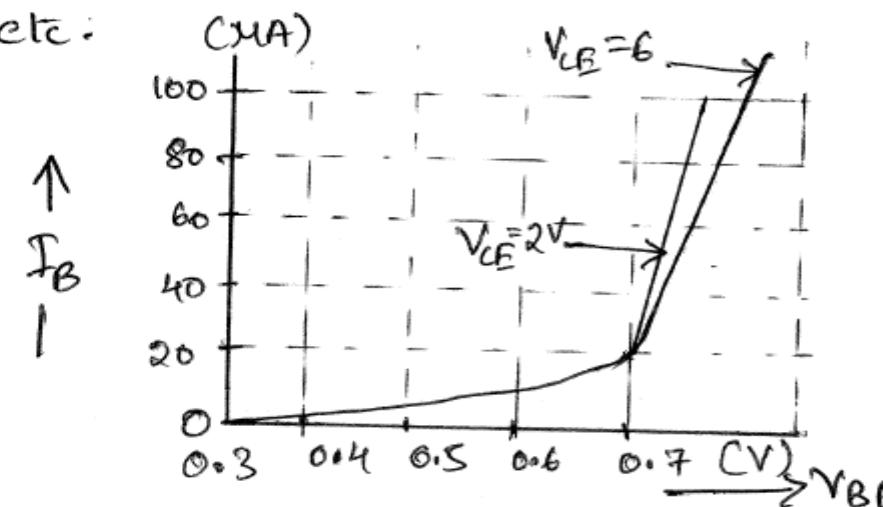



- * I_{BP} resistance is defined as the ratio of change in base-emitter voltage 'AV_{BE}' to the resulting change in base-current 'ΔI_B' at constant collector-emitter voltage.

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B} \quad | V_{CE} \text{ constant}$$


(600Ω to 400Ω)

- * fig ⑤ shows that, for a given level of V_{BE}, I_B is reduced when higher V_{CE} levels are employed. This is because higher 'V_{CE}' produces greater depletion region penetration into the base, reducing the distance b/w the CB & EB depletion regions.



- * Thus more of the charge moves from the emitter flow across the CB-Junction & less current flow from base terminal.

O/P characteristics :-

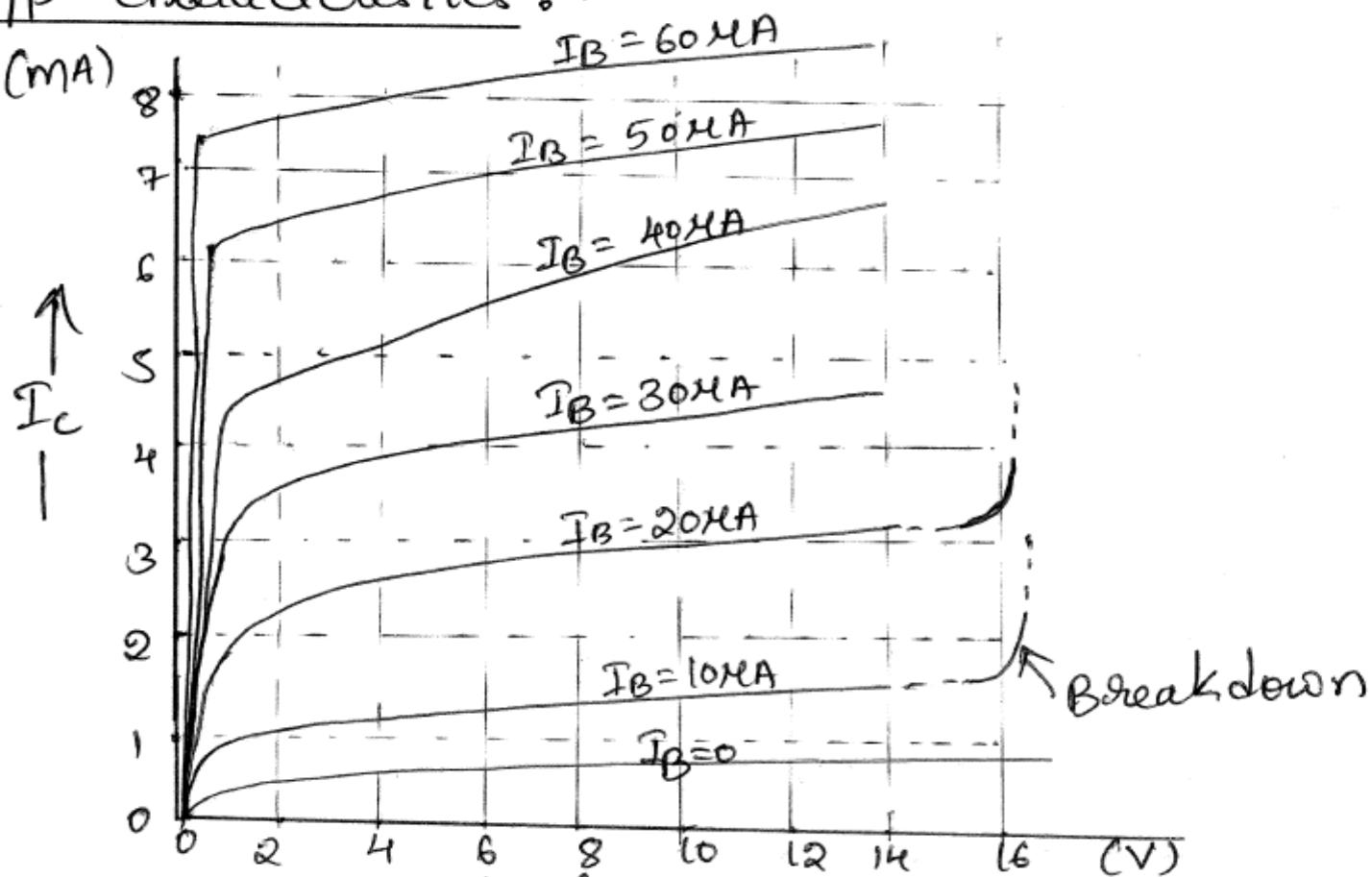



- * By using base-emitter voltage ' V_{BE} ' , ' I_B ' is maintained constant at several convenient levels.
- * ' V_{CE} ' is varied in suitable steps & at each step I_C value is recorded. The same procedure is repeated for different settings of I_B .
- * If we plot a graph with ' V_{CE} ' voltage along horizontal axis & the collector current ' I_C ' along the vertical axis , we shall obtain a o/p characteristic as shown in fig ③.
- * o/p resistance ' r_o ' is defined as the ratio of change in collector to emitter voltage ' ΔV_{CE} ' to the resulting change in collector current ' ΔI_C ' at constant base current ' I_B '.

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C} \mid_{I_B \text{ constant}}$$

(10k Ω to 50k Ω)




- * The o/p characteristic curve is divided into 3 regions namely:
 - 1) Saturation region.
 - 2) Active region.
 - 3) cut-off region.
- i) In saturation region, when the collector to emitter voltage ' V_{CE} ' is increased above zero, the collector current ' I_C ' increases rapidly to a saturation value, depending upon the value of base current.
- * It may be noted that collector current I_C reaches to a Saturation value when V_{CE} is about 0.5V.
- i) In active region, the collector current is β_{de} times greater than the base current. Thus small I/F current ' I_B ' produces a large o/p current I_C .
- i) In cutoff region, when base current is zero ($I_B=0$), collector current is not zero ($I_C \neq 0$), a small collector current exists called reverse leakage current ' I_{CEO} '.




Current Gain :-

Current gain characteristics (mA)

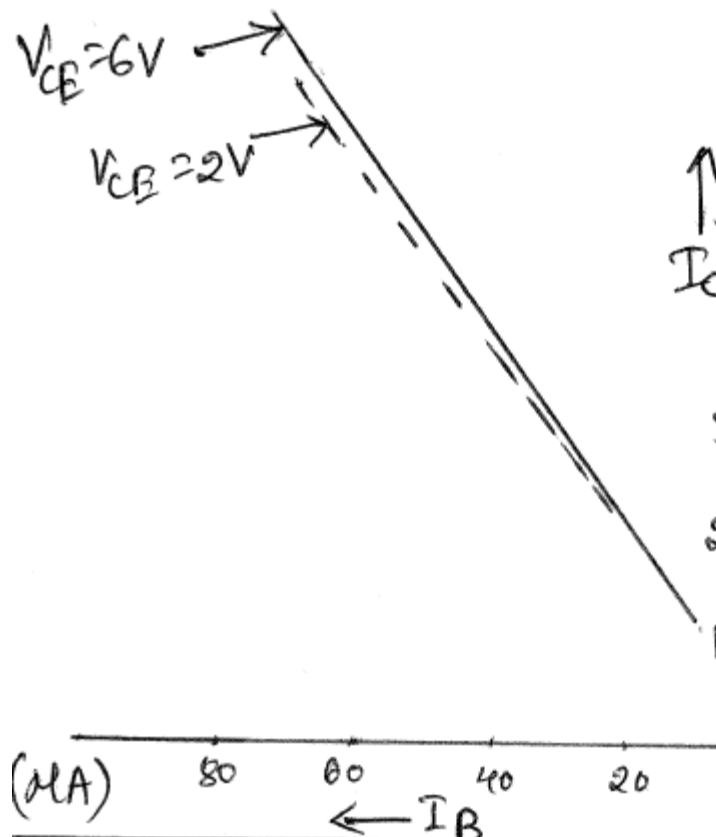

Output characteristics

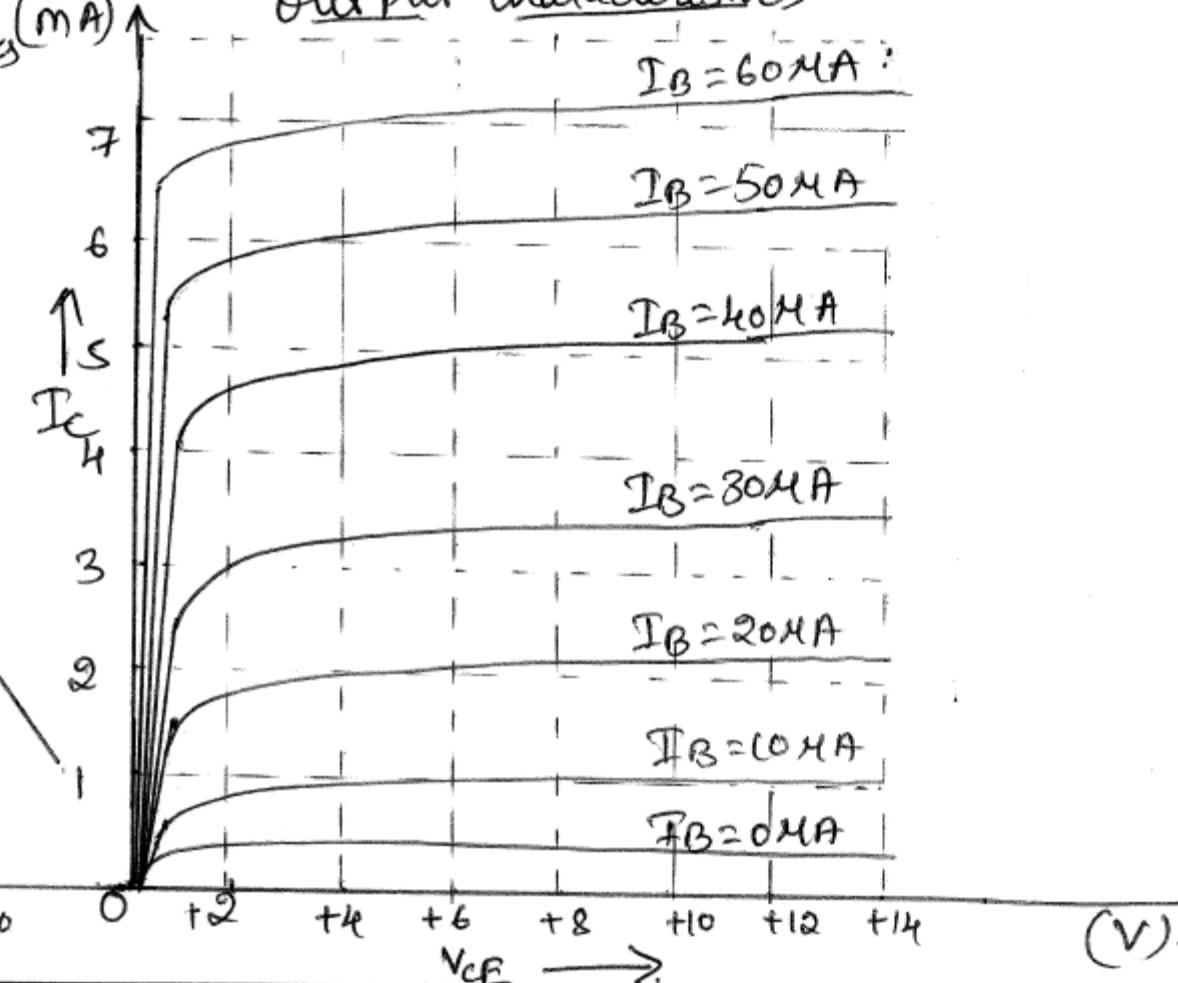



- * Common emitter current gain characteristics shows the variation of I_c as a function of I_B with constant ' V_{CE} '. i.e. ' V_{CE} ' is held at a convenient level & I_B is varied in suitable steps and at each step I_c value is recorded. I_c is then plotted as a function of I_B .
- * A vertical line is drawn through a selected V_{CE} value & the corresponding levels of I_c & I_B are read along the line.



* calculate α_{dc} and β_{dc} for the transistor if I_c is measured as 1mA and I_B is 25μA. Also determine the new base current to give $I_c = 5\text{mA}$.

June - 08, 6M1

Given :- (i) $I_c = 1\text{mA}$, $I_B = 25\mu\text{A}$, $\alpha_{dc} = ?$ $\beta_{dc} = ?$

(ii) $I_c = 5\text{mA}$, $I_B = ?$

Sol :-

$$\text{i)} * \beta_{dc} = \frac{I_c}{I_B} = \frac{1\text{mA}}{25\mu\text{A}} = 40.$$

$$* \alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}} = \frac{40}{1 + 40} = 0.9756.$$

ii) When $I_c = 5\text{mA}$

$$* I_B = \frac{I_c}{\beta_{dc}} = \frac{5\text{mA}}{40} = 125\mu\text{A}.$$



* Calculate the values of I_c , I_E and β_{dc} for a transistor with $\alpha_{dc} = 0.98$ and $I_B = 120 \mu A$.

Jan-09, 4M

Given: $\alpha_{dc} = 0.98$, $I_B = 120 \mu A$, $I_c = ?$, $I_E = ?$ & $\beta_{dc} = ?$.

Sol:

$$* \beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}} = \frac{0.98}{1 - 0.98} = 49$$

$$* I_c = \beta_{dc} I_B = 49 \times 120 \mu A = 5.88 \text{ mA.}$$



* Given $I_E = 2.5 \text{ mA}$, $\alpha = 0.98$ and $I_{CBO} = 10 \mu\text{A}$, calculate I_B and I_C

Jan - II, 4M

Sol:-

WKT. $\alpha = \frac{I_C}{I_E}$

$$I_C = \alpha I_E = 0.98 \times 2.5 \text{ mA}$$

$$I_C = 2.45 \text{ mA}$$

WKT. $I_E = I_B + I_C$

$$I_B = I_E - I_C = 2.5 \text{ mA} - 2.45 \text{ mA}$$

$$I_B = 50 \mu\text{A}$$



{ calculate I_c & I_E for a transistor that has $\alpha_{dc} = 0.98$ & $I_B = 100 \mu A$. Also determine the value of B_{dc} for the transistor. (Reference book).

Sol:

$$* I_c = \frac{\alpha_{dc}}{1 - \alpha_{dc}} I_B = \frac{0.98}{1 - 0.98} * 100 \mu A = 4.9 \text{ mA}$$

$$* I_c = \alpha_{dc} I_E,$$

$$I_E = \frac{I_c}{\alpha_{dc}} = \frac{4.9 \text{ mA}}{0.98} = 5 \text{ mA}$$

$$* B_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}} = \frac{0.98}{1 - 0.98} = 49.$$



2) calculate α_{dc} & β_{dc} for the transistor in fig ① if I_c is measured as 1mA, & I_B is 25 μA. Also determine the new base current to give $I_c = 5\text{mA}$.


SOL: * $\beta_{dc} = \frac{I_c}{I_B} = \frac{1\text{mA}}{25\text{μA}} = 40$

* $I_E = I_B + I_c = 1\text{mA} + 25\text{μA}$
 $= 1.025\text{mA}$

* $\alpha_{dc} = \frac{I_c}{I_E} = \frac{1\text{mA}}{1.025\text{mA}} = 0.976$

* New base current to give $I_c = 5\text{mA}$
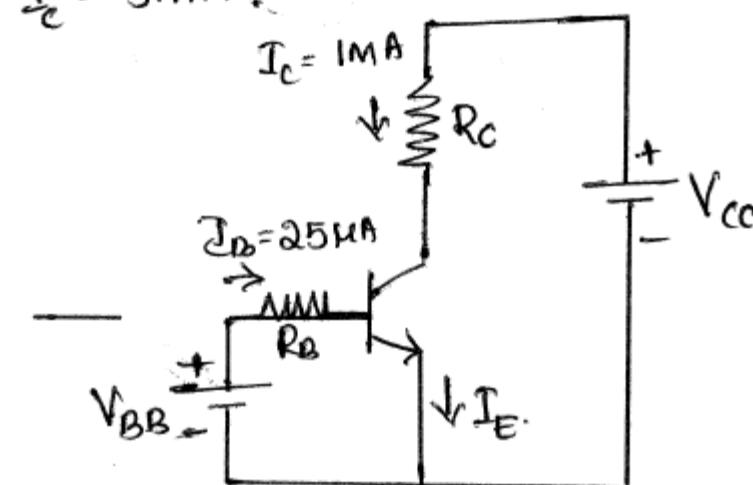
$$I_B = I_c / \beta_{dc} = 5\text{mA} / 40 = \underline{\underline{125\text{μA}}}$$



(Reference book)



3) A transistor has $I_B = 100 \mu A$ & $I_C = 2mA$, find

- i) β of the transistor.
- ii) α of the transistor.
- iii) emitter current I_E
- iv) If I_B changes by $+25 \mu A$ & I_C changes by $+0.6 mA$.
find the new value of β .

July 06, 10 M

Sol:- Given : $I_B = 100 \mu A$ & $I_C = 2mA$;

$$\text{i)} \quad \beta = \frac{I_C}{I_B} = \frac{2mA}{100 \mu A} = \frac{2mA}{100 \mu A} = 20$$

$$\text{ii)} \quad \alpha = \frac{\beta}{1+\beta} = \frac{20}{1+20} = 0.952$$

$$\text{iii)} \quad I_E = I_B + I_C = 100 \mu A + 2mA = 2.1mA$$

$$\text{iv)} \quad \text{New } I_B = 100 \mu A + 25 \mu A = 125 \mu A$$

$$\text{New } I_C = 2mA + 0.6 mA = 2.6 mA$$

$$\text{New } \beta = \frac{2.6mA}{125 \mu A} = 20.8$$



4. If α for a transistor is 0.99, the base current is $100 \mu A$, estimate the collector current.

March - 99, 5M

Sol: Given $I_B = 100 \mu A$, $\alpha = 0.99$

WKT. $\beta = \frac{I_C}{I_B}$ & $\beta = \frac{\alpha}{1-\alpha}$

$$\beta = \frac{0.99}{1-0.99} = \underline{\underline{99}}$$

$$I_C = \beta I_B \\ = 99 \times 100 \mu A$$

$I_C = 9.9 \text{ mA}$



5) For a transistor $I_E = 1\text{mA}$, $I_B = 10\text{\mu A}$, determine α & β .

Sol: $I_E = 1\text{mA}$, $I_B = 10\text{\mu A}$.

March - 2001, 5M

WKT.

$$I_E = I_B + I_C$$

$$= I_B + \beta I_B$$

$$I_E = I_B [1 + \beta]$$

$$[1 + \beta] = \frac{I_E}{I_B} = \frac{1\text{mA}}{10\text{\mu A}} = 100$$

$$1 + \beta = 100$$

$$\beta = 99$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{99}{1 + 99} = \underline{\underline{0.99}}$$



6) A transistor amplifier connected in CE mode has
 $\beta = 100$ & $I_B = 50 \mu A$. Compute the values of I_C , I_E & α_c .

Sol: Given : $\beta = 100$, $I_B = 50 \mu A$

feb - 2002, 5M

$$I_C = \beta I_B = (100)(50 \mu A) = 5mA$$

also,
$$\boxed{\beta = \frac{I_C}{I_B}}$$

$$I_E = I_B + I_C = 5mA + 50 \mu A = 5.05mA.$$

$$\alpha_c = \frac{\beta}{1+\beta} = \frac{100}{1+100} = 0.99.$$



10) In a certain transistor, 99.6% of the carriers injected into the base cross the collector-base junction. If the leakage current is 5μA, & the collector current is 20mA, calculate (i) the value of α_{dc} (ii) The emitter current.

Sol: Given : $I_c = 0.996 I_E$, $I_{CBO} = 5\mu A$, $I_c = 20mA$.

i) $\alpha_{dc} = \frac{I_c}{I_E} = \underline{\underline{0.996}}$. i.e. $I_c = \alpha_{dc} \cdot I_E$.

ii) W.K.T. $I_c = \overbrace{\alpha_{dc} I_E + I_{CBO}}$.

$$\boxed{\alpha_{dc} = \frac{I_c}{I_E}}$$

$$I_c - I_{CBO} = \alpha_{dc} I_E$$

$$I_E = \frac{I_c - I_{CBO}}{\alpha_{dc}} = \frac{20mA - 5\mu A}{0.996} = \underline{\underline{20.07mA}}$$



11) Find α_{dc} , I_B & β_{dc} for transistor with $I_c = 2.5\text{mA}$ &
 $I_E = 2.55\text{mA}$.

Sol: Given : $I_c = 2.5\text{mA}$, $I_E = 2.55\text{mA}$.

$$* \alpha_{dc} = \frac{I_c}{I_E} = \frac{2.5\text{mA}}{2.55\text{mA}} = 0.9804$$

$$* \overbrace{I_E}^{\leftarrow} = I_B + I_C$$

$$I_B = I_E - I_C = 2.55\text{mA} - 2.5\text{mA} = 50\text{mA}$$

$$* \beta_{dc} = \frac{I_c}{I_B} = \frac{2.5\text{mA}}{0.05\text{mA}} = 50$$

$$* \beta_{dc} = \frac{\alpha}{1-\alpha} = \frac{0.9804}{1-0.9804} = 50$$

FEEDBACK



- In the feedback process a part of output is sampled and fed back to the input.
- The fed back signal can be in phase with or out of phase with the original input signal.

Definition of feedback:

- Feedback is defined as the process in which a part of output signal (voltage or current) is returned back to the input.
- The amplifier that operates on the principle of feedback is known as feedback amplifier.

TYPES OF FEEDBACK


1. Positive feedback
2. Negative feedback.

If the original input signal and the feedback signal are in phase, the feedback is called as positive feedback.

However if these two signals are out of phase then the feedback is called as negative feedback.



AMPLIFIER WITHOUT FEEDBACK

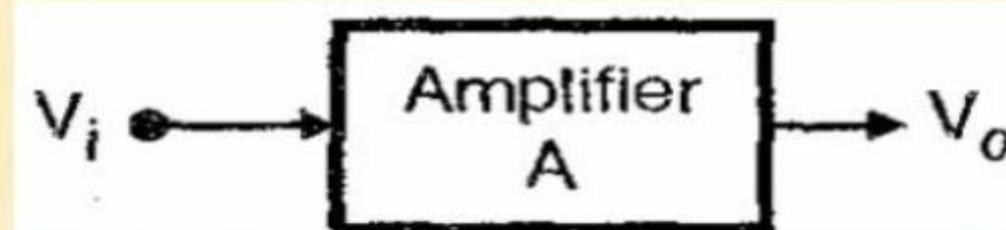


- The most important thing to understand from Fig. is that the output and input terminals of this amplifier are not connected to each other in any way.
- Therefore the amplifier of Fig. is an amplifier without any feedback,

Gain without feedback.

$$A = \frac{V_o}{V_i}$$

AMPLIFIER WITH FEEDBACK

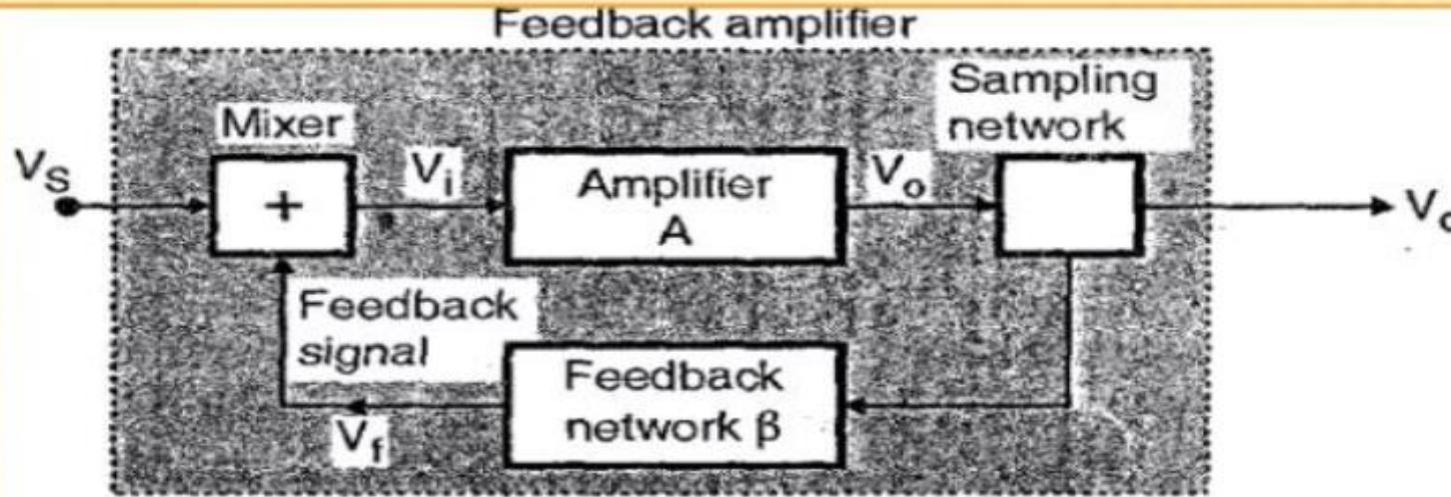


- Refer to Fig. Here the same amplifier with a gain A is being used along with a mixer network, sampling network and a feedback network.
- The voltage gain of the feedback amplifier is given by,

Gain with feedback

$$A_f = \frac{V_o}{V_s}$$



AMPLIFIER WITH A NEGATIVE FEEDBACK

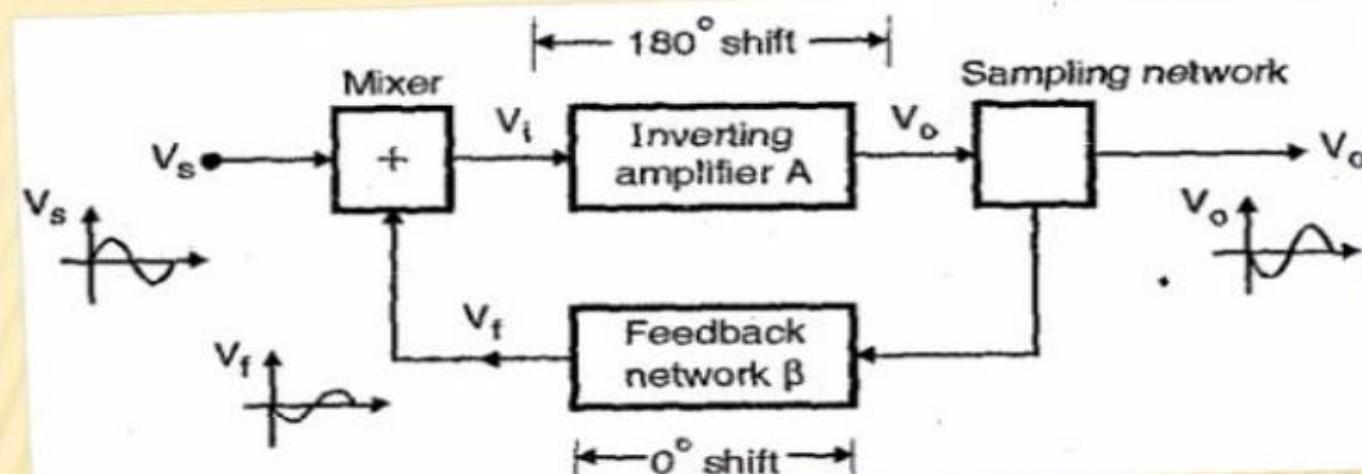

- The block diagram of an amplifier with a Negative Feedback Fig.

$$V_f = \beta V_o$$

Where V_f = Feedback signal (output of the feedback network)

$$\text{Feedback factor } \beta = \frac{V_f}{V_o}$$

TYPES OF NEGATIVE FEEDBACK:

- Depending on the type of sampling and mixing networks, the feedback amplifiers are classified into four categories:
- Voltage series feedback
- Current series feedback
- Current shunt feedback
- Voltage shunt feedback




VOLTAGE SERIES FEEDBACK

Therefore,

voltage series feedback = voltage sampling + series mixing

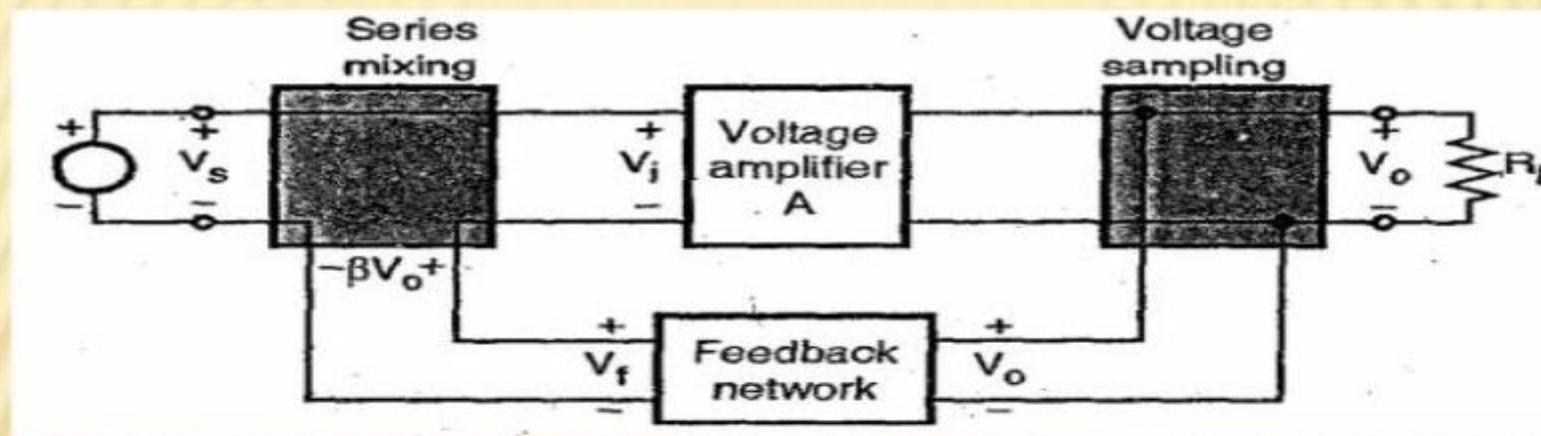The voltage series feedback is present in the voltage amplifiers.



A transistor amplifier which uses the voltage series feedback is the common collector or emitter follower amplifier:


1. A common collector (or emitter follower) amplifier using BJT.
2. A common drain (or source follower) amplifier using FET.



CURRENT SERIES FEEDBACK

Therefore

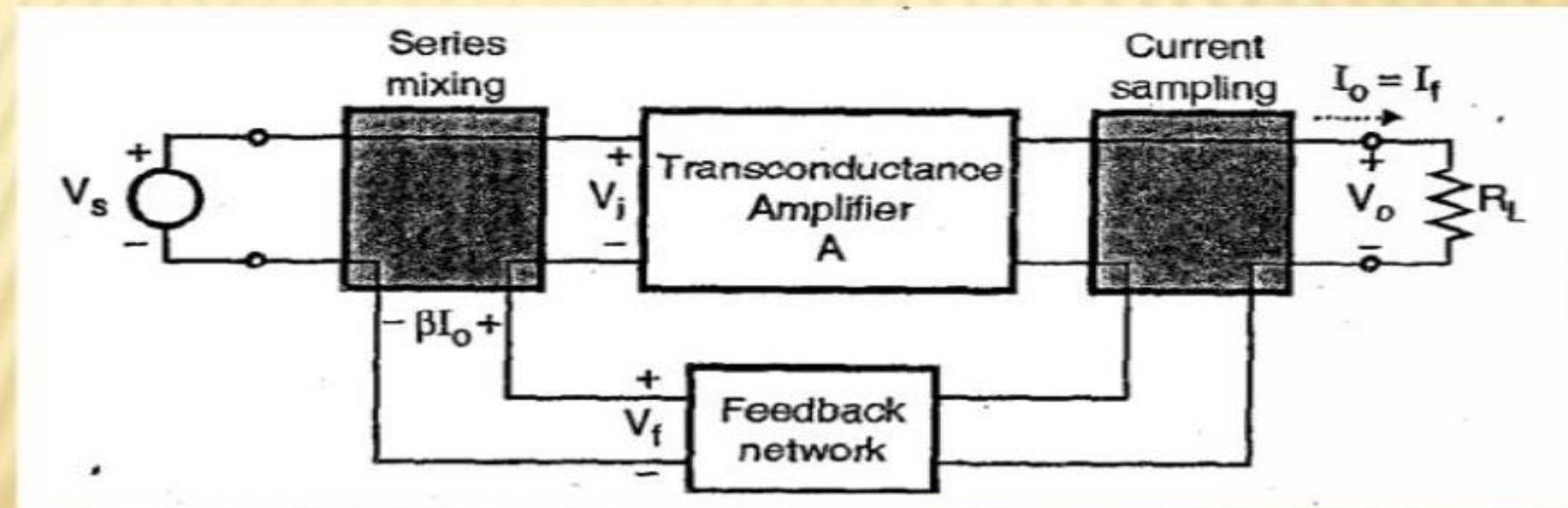- Current sampling + Series mixing.
- Current series feedback is present in the transconductance amplifiers






CURRENT SHUNT FEEDBACK:

- This is a combination of current sampling and shunt mixing. The block diagram of a feedback amplifier with current shunt feedback is shown in Fig.

Current sampling + Shunt mixing

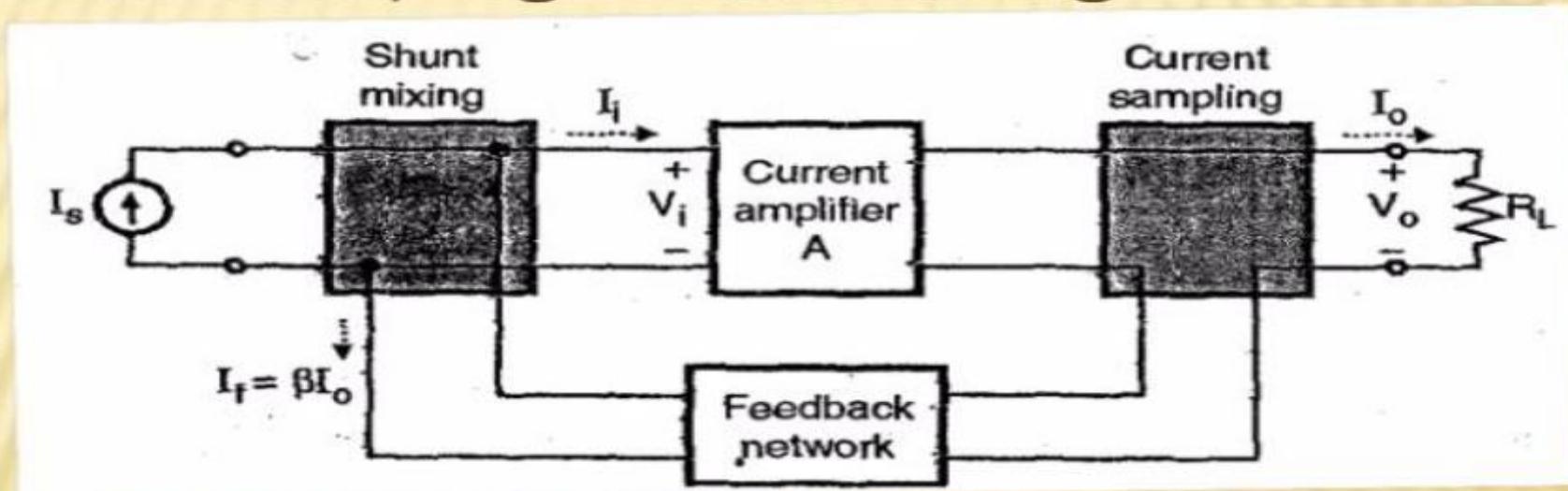

- Current shunt feedback is present in the current amplifiers.




VOLTAGE SHUNT FEEDBACK

- The block diagram of an amplifier with voltage shunt feedback amplifier is shown in Fig.

Voltage Shunt Feedback = Voltage Sampling + Shunt Mixing.

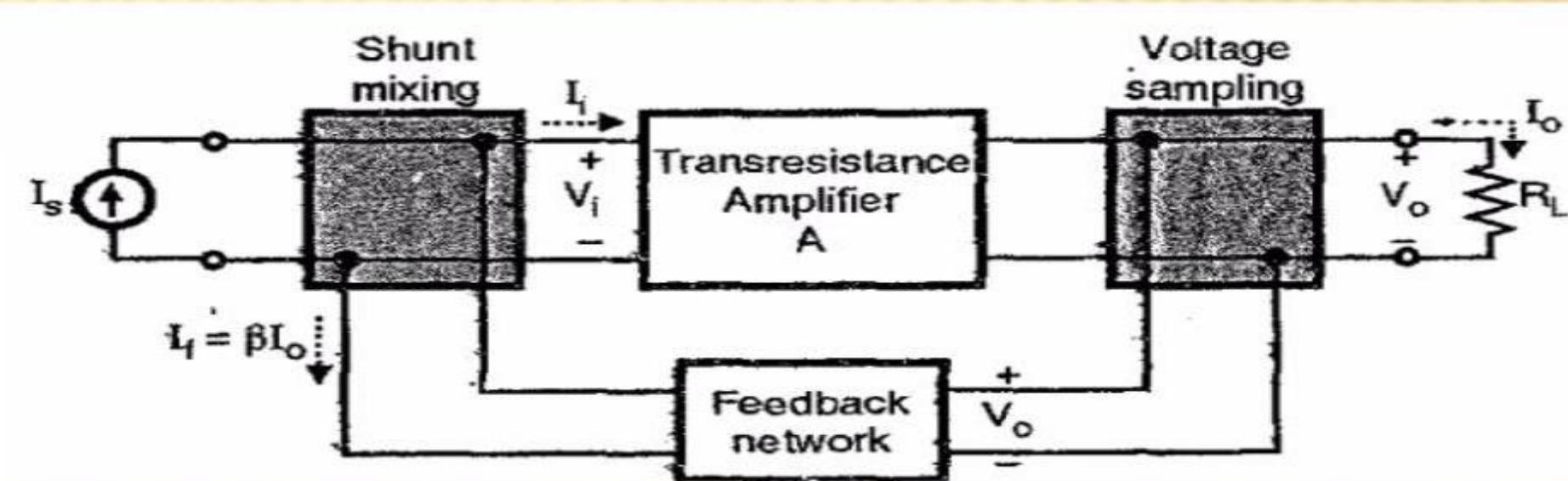- The voltage shunt feedback is present in the transresistance amplifier.





ADVANTAGES & DISADVANTAGES

Advantages

- Negative feedback stabilizes the gain of the amplifier.
- Input resistance increases for certain feedback configurations.
- Output resistance decreases for certain feedback configurations.
- Operating point is stabilized.

Disadvantages

- Reduction in gain.
- Reduction in input resistance in case of voltage shunt and current shunt type amplifiers.
- Increase in output resistance in case of current shunt and current series feedback amplifiers.

Applications of negative feedback

- In almost all the electronic amplifiers.
- In the regulated power supplies.
- In wideband amplifiers (amplifiers having a large bandwidth)